

Problem: ripple carry adder is slow

- Is a 32-bit ALU as fast as a 1-bit ALU?
- Is there more than one way to do addition?
 - two extremes: ripple carry and sum-of-products

Can you see the ripple? How could you get rid of it?

$$\begin{aligned}c_1 &= b_0c_0 + a_0c_0 + a_0b_0 \\c_2 &= b_1c_1 + a_1c_1 + a_1b_1 & c_2 &= \\c_3 &= b_2c_2 + a_2c_2 + a_2b_2 & c_3 &= \\c_4 &= b_3c_3 + a_3c_3 + a_3b_3 & c_4 &= \end{aligned}$$

Not feasible! Why?



Carry-lookahead adder

- An approach in-between our two extremes
- Motivation:
 - If we didn't know the value of carry-in, what could we do?
 - When would we always generate a carry?
 - When would we propagate the carry?
- Did we get rid of the ripple?


$$\begin{aligned}g_i &= a_i b_i \\p_i &= a_i + b_i\end{aligned}$$

$$\begin{aligned}c_1 &= g_0 + p_0c_0 \\c_2 &= g_1 + p_1c_1 & c_2 &= \\c_3 &= g_2 + p_2c_2 & c_3 &= \\c_4 &= g_3 + p_3c_3 & c_4 &= \end{aligned}$$

Feasible! Why?

  


Use principle to build bigger adders

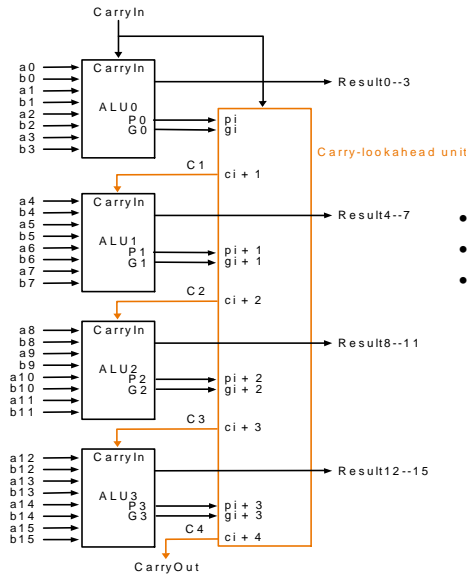


- Can't build a 16 bit adder this way... (too big)
- Could use ripple carry of 4-bit CLA adders
- Better: use the CLA principle again!

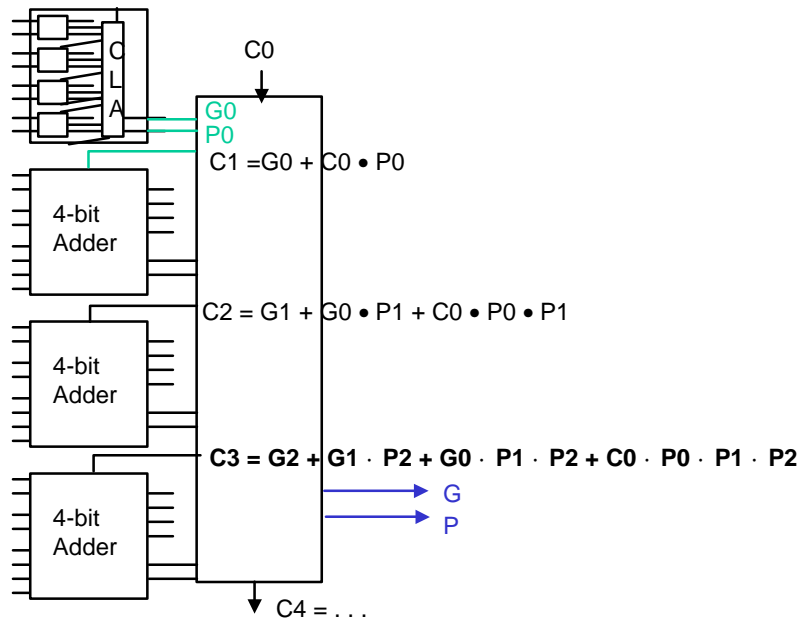Cascaded Carry Look-ahead (16-bit): Abstraction



2nd level Carry, Propagate as Plumbing

 

MIPS arithmetic instructions

<i>Instruction</i>	<i>Example</i>	<i>Meaning</i>	<i>Comments</i>
add	add \$1,\$2,\$3	$S1 = S2 + S3$	3 operands; exception possible
subtract	sub \$1,\$2,\$3	$S1 = S2 - S3$	3 operands; exception possible
add immediate	addi \$1,\$2,100	$S1 = S2 + 100$	+ constant; exception possible
add unsigned	addu \$1,\$2,\$3	$S1 = S2 + S3$	3 operands; no exceptions
subtract unsigned	subu \$1,\$2,\$3	$S1 = S2 - S3$	3 operands; no exceptions
add imm. unsign.	addiu \$1,\$2,100	$S1 = S2 + 100$	+ constant; no exceptions
multiply	mult \$2,\$3	Hi, Lo = $S2 \times S3$	64-bit signed product
multiply unsigned	multu \$2,\$3	Hi, Lo = $S2 \times S3$	64-bit unsigned product
divide	div \$2,\$3	Lo = $S2 \div S3$, Hi = $S2 \bmod S3$	Lo = quotient, Hi = remainder
divide unsigned	divu \$2,\$3	Lo = $S2 \div S3$, Hi = $S2 \bmod S3$	Unsigned quotient & remainder
Move from Hi	mfhi \$1	$S1 = \text{Hi}$	Used to get copy of Hi
Move from Lo	mflo \$1	$S1 = \text{Lo}$	Used to get copy of Lo

MULTIPLY (unsigned)

Paper and pencil example (unsigned):

Multiplicand	1000
Multiplier	1001
	<hr/>
	1000
	0000
	0000
	1000
	<hr/>
Product	01001000

m bits x n bits = m+n bit product

Binary makes it easy:


0 => place 0 (0 x multiplicand)

1 => place a copy (1 x multiplicand)

3 versions of multiply hardware & algorithm:


[successive refinement](#)

Unsigned Combinational Multiplier

 

- Stage i accumulates $A * 2^i$ if $B_i == 1$


How does it work?

 

- at each stage shift A left (x 2)
- use next bit of B to determine whether to add in shifted multiplicand
- accumulate 2n bit partial product at each stage


Unsigned shift-add multiplier (version 1)

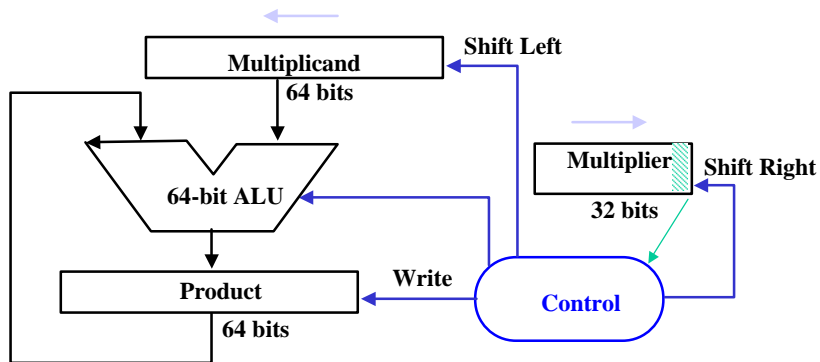- 64-bit Multiplicand reg, 64-bit ALU, 64-bit Product reg, 32-bit multiplier reg



Multiplier = datapath + control

Multiply Algorithm Version 1

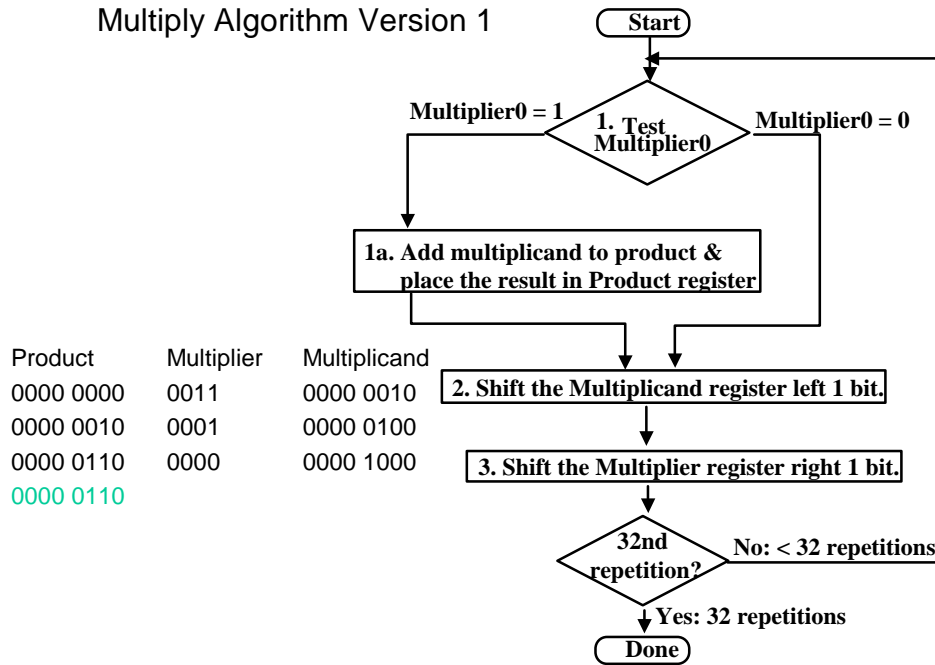


	M'ier: 0011	M'and: 0000 0010	P: 0000 0000
1a. 1=>P=P+Mcand	M'ier: 0011	Mcand: 0000 0010	P: <u>0000 0010</u>
2. Shl Mcand	M'ier: 0011	<u>Mcand: 0000 0100</u>	P: 0000 0010
3. Shr M'ier	<u>M'ier: 0001</u>	Mcand: 0000 0100	P: 0000 0010
1a. 1=>P=P+Mcand	M'ier: 0001	Mcand: 0000 0100	P: <u>0000 0110</u>
2. Shl Mcand	M'ier: 0001	<u>Mcand: 0000 1000</u>	P: 0000 0110
3. Shr M'ier	<u>M'ier: 0000</u>	Mcand: 0000 1000	P: 0000 0110
1. 0=>nop	M'ier: 0000	Mcand: 0000 1000	P: 0000 0110
2. Shl Mcand	M'ier: 0000	<u>Mcand: 0001 0000</u>	P: 0000 0110
3. Shr M'ier	<u>M'ier: 0000</u>	Mcand: 0001 0000	P: 0000 0110
1. 0=>nop	M'ier: 0000	Mcand: 0001 0000	P: 0000 0110
2. Shl Mcand	M'ier: 0000	<u>Mcand: 0010 0000</u>	P: 0000 0110
3. Shr M'ier	<u>M'ier: 0000</u>	Mcand: 0010 0000	P: 0000 0110

Observations on Multiply Version 1


- 1/2 bits in multiplicand always 0
=> 64-bit adder is wasted
- 0's inserted in left of multiplicand as shifted
=> least significant bits of product never changed once formed
- Instead of shifting multiplicand to left, shift product to right?

MULTIPLY HARDWARE Version 2

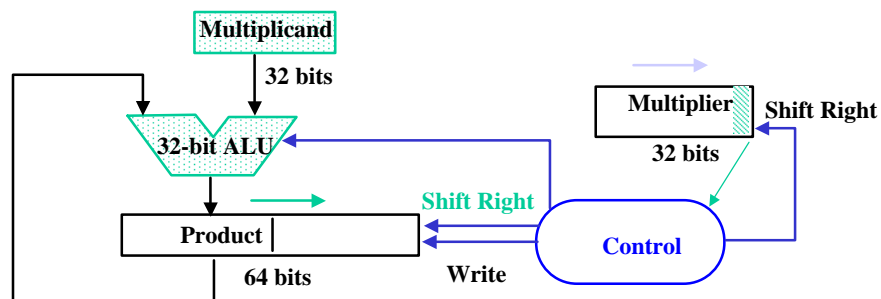- 32-bit Multiplicand reg, 32-bit ALU, 64-bit Product reg, 32-bit Multiplier reg




Multiply Algorithm Version 2

 

	M'ier: 0011	Mcand: 0010	P: 0000 0000
1a. 1=>P=P+Mcand	M'ier: 0011	Mcand: 0010	P: <u>0010</u> 0000
2. Shr P	M'ier: 0011	Mcand: 0010	P: <u>0001</u> <u>0000</u>
3. Shr M'ier	<u>M'ier: 0001</u>	Mcand: 0010	P: 0001 0000
1a. 1=>P=P+Mcand	M'ier: 0001	Mcand: 0010	P: <u>0011</u> 0000
2. Shr P	M'ier: 0001	Mcand: 0010	P: <u>0001</u> <u>1000</u>
3. Shr M'ier	<u>M'ier: 0000</u>	Mcand: 0010	P: 0001 1000
1. 0=>nop	M'ier: 0000	Mcand: 0010	P: 0001 1000
2. Shr P	M'ier: 0000	Mcand: 0010	P: <u>0000</u> <u>1100</u>
3. Shr M'ier	<u>M'ier: 0000</u>	Mcand: 0010	P: 0000 1100
1. 0=>nop	M'ier: 0000	Mcand: 0010	P: 0000 1100
2. Shr P	M'ier: 0000	Mcand: 0010	P: <u>0000</u> <u>0110</u>
3. Shr M'ier	<u>M'ier: 0000</u>	Mcand: 0010	P: 0000 0110

What's going on?

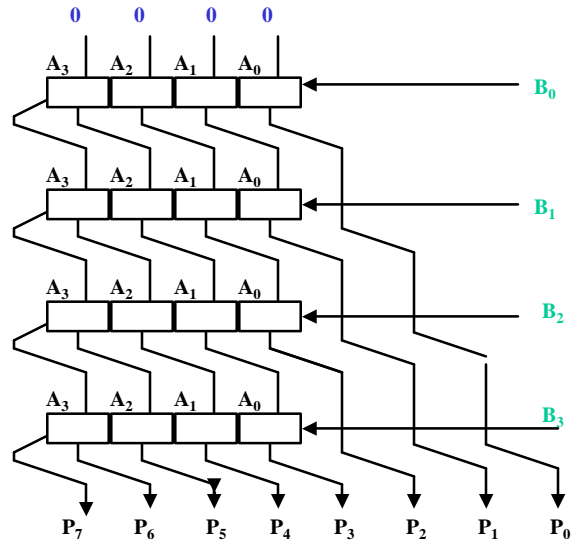


- Multiplicand stays still and product moves right

Break

- 5-minute Break/ Do it yourself Multiply

Multiplier	Multiplicand	Product
0011	0010	0000 0000

Multiply Algorithm Version 2

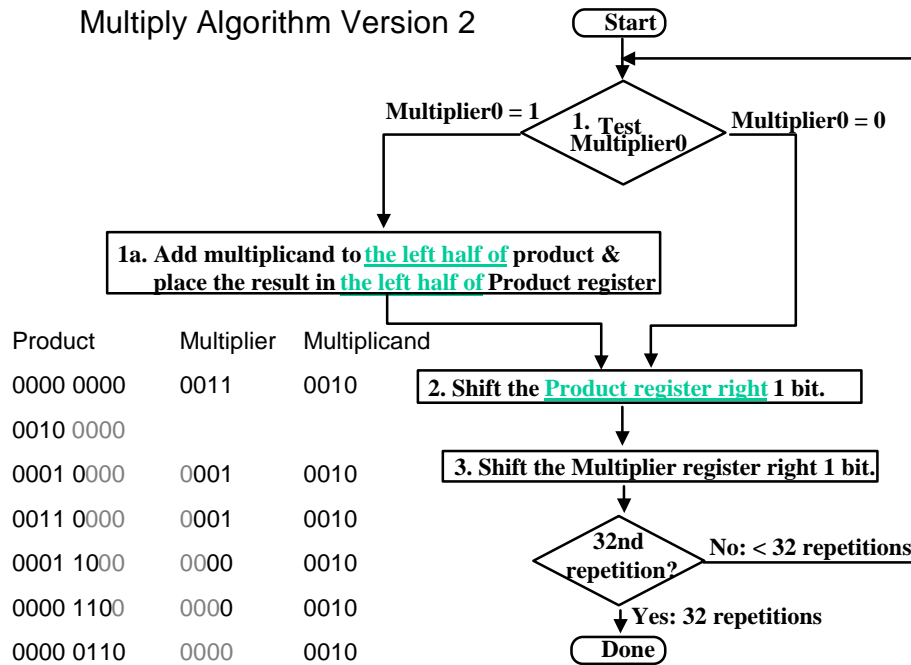


	M'ier: 0011	Mcand: 0010	P: 0000 0000
1a. 1=>P=P+Mcand	M'ier: 0011	Mcand: 0010	P: <u>0010</u> 0000
2. Shr P	M'ier: 0011	Mcand: 0010	P: <u>0001</u> <u>0000</u>
3. Shr M'ier	<u>M'ier: 0001</u>	Mcand: 0010	P: 0001 0000
1a. 1=>P=P+Mcand	M'ier: 0001	Mcand: 0010	P: <u>0011</u> 0000
2. Shr P	M'ier: 0001	Mcand: 0010	P: <u>0001</u> <u>1000</u>
3. Shr M'ier	<u>M'ier: 0000</u>	Mcand: 0010	P: 0001 1000
1. 0=>nop	M'ier: 0000	Mcand: 0010	P: 0001 1000
2. Shr P	M'ier: 0000	Mcand: 0010	P: <u>0000</u> <u>1100</u>
3. Shr M'ier	<u>M'ier: 0000</u>	Mcand: 0010	P: 0000 1100
1. 0=>nop	M'ier: 0000	Mcand: 0010	P: 0000 1100
2. Shr P	M'ier: 0000	Mcand: 0010	P: <u>0000</u> <u>0110</u>
3. Shr M'ier	<u>M'ier: 0000</u>	Mcand: 0010	P: 0000 0110

Observations on Multiply Version 2

- Product register wastes space that exactly matches size of multiplier
=> combine Multiplier register and Product register


MULTIPLY HARDWARE Version 3

 - 32-bit Multiplicand reg, 32-bit ALU, 64-bit Product reg, (0-bit Multiplier reg)



Multiply Algorithm Version 3

Multiplicand Product
 0010 0000 0011

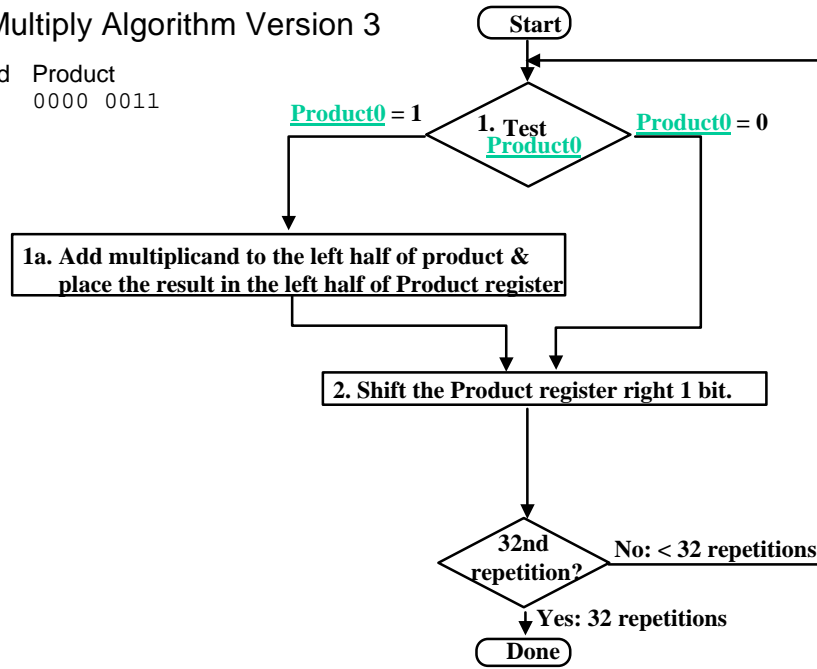

Mcand: 0010

P: 0000 0011

1a. 1=>P=P+Mcand

Mcand: 0010 P: 0010 0011

2. Shr P

Mcand: 0010 P: 0001 0001

1a. 1=>P=P+Mcand

Mcand: 0010 P: 0011 0001

2. Shr P

Mcand: 0010 P: 0001 1000

1. 0=>nop

Mcand: 0010 P: 0001 1000

2. Shr P

Mcand: 0010 P: 0000 1100

1. 0=>nop

Mcand: 0010 P: 0000 1100

2. Shr P

Mcand: 0010 P: 0000 0110

Observations on Multiply Version 3

- 2 steps per bit because Multiplier & Product combined
- MIPS registers Hi and Lo are left and right half of Product
- Gives us MIPS instruction MultU
- How can you make it faster?
- What about signed multiplication?
 - easiest solution is to make both positive & remember whether to complement product when done (leave out the sign bit, run for 31 steps)
 - apply definition of 2's complement
 - need to sign-extend partial products and subtract at the end
 - Booth's Algorithm is elegant way to multiply signed numbers using same hardware as before and save cycles
 - can handle multiple bits at a time

MIPS logical instructions

<i>Instruction</i>	<i>Example</i>	<i>Meaning</i>	<i>Comment</i>
and	and \$1,\$2,\$3	$\$1 = \$2 \& \$3$	3 reg. operands; Logical AND
or	or \$1,\$2,\$3	$\$1 = \$2 \$3$	3 reg. operands; Logical OR
xor	xor \$1,\$2,\$3	$\$1 = \$2 \oplus \$3$	3 reg. operands; Logical XOR
nor	nor \$1,\$2,\$3	$\$1 = \sim(\$2 \$3)$	3 reg. operands; Logical NOR
and immediate	andi \$1,\$2,10	$\$1 = \$2 \& 10$	Logical AND reg, constant
or immediate	ori \$1,\$2,10	$\$1 = \$2 10$	Logical OR reg, constant
xor immediate	xori \$1, \$2,10	$\$1 = \sim\$2 \& \sim 10$	Logical XOR reg, constant
shift left logical	sll \$1,\$2,10	$\$1 = \$2 \ll 10$	Shift left by constant
shift right logical	srl \$1,\$2,10	$\$1 = \$2 \gg 10$	Shift right by constant
shift right arithm.	sra \$1,\$2,10	$\$1 = \$2 \gg 10$	Shift right (sign extend)
shift left logical	sllv \$1,\$2,\$3	$\$1 = \$2 \ll \$3$	Shift left by variable
shift right logical	srlv \$1,\$2, \$3	$\$1 = \$2 \gg \$3$	Shift right by variable
shift right arithm.	srav \$1,\$2, \$3	$\$1 = \$2 \gg \$3$	Shift right arith. by variable


Shifters

Two kinds:

logical-- value shifted in is always "0"



 arithmetic-- on right shifts, sign extend



Note: these are single bit shifts. A given instruction might request 0 to 32 bits to be shifted!

Floating-Point


What can be represented in N bits?

- Unsigned 0 to 2^N
- 2s Complement -2^{N-1} to $2^{N-1} - 1$
- But, what about?
 - very large numbers?
9,349,398,989,787,762,244,859,087,678
 - very small number?
0.000000000000000000000045691
 - rationals $\frac{2}{3}$
 - irrationals $\sqrt{2}$
 - transcendentals e, π

Floating Point

- We need a way to represent
 - numbers with fractions, e.g., 3.1416
 - very small numbers, e.g., .000000001
 - very large numbers, e.g., 3.15576×10^9
- Representation:
 - sign, exponent, significand: $(-1)^{\text{sign}} \times \text{significand} \times 2^{\text{exponent}}$
 - more bits for significand gives more accuracy
 - more bits for exponent increases range
- IEEE 754 floating point standard:
 - single precision: 8 bit exponent, 23 bit significand
 - double precision: 11 bit exponent, 52 bit significand

Recall Scientific Notation

 

IEEE F.P. $\pm 1.M \times 2^{\text{e} - 127}$


- Issues:
 - Arithmetic (+, -, *, /)
 - Representation, Normal form
 - Range and Precision
 - Rounding
 - Exceptions (e.g., divide by zero, overflow, underflow)
 - Errors
 - Properties (negation, inversion, if $A < B$ then $A - B < 0$)

IEEE 754 floating-point standard

- Leading “1” bit of significand is implicit
- Exponent is “biased” to make sorting easier
 - all 0s is smallest exponent all 1s is largest
 - bias of 127 for single precision and 1023 for double precision
 - summary: $(-1)^{\text{sign}} \times (1 + \text{significand}) \times 2^{\text{exponent} - \text{bias}}$
- Example:
 - decimal: $-.75 = -3/4 = -3/2^2$
 - binary: $-.11 = -1.1 \times 2^{-1}$
 - floating point: exponent = 126 = 01111110
 - IEEE single precision: 10111111010000000000000000000000

IEEE 754 Standard

 Representation of floating point numbers in IEEE 754 standard:



exponent:
bias 127
binary integer

mantissa:
sign + magnitude, normalized
binary significand w/ hidden
integer bit: 1.M

actual exponent is
 $e = E - 127$

$0 < E < 255$

$$N = (-1)^S 2^{E-127} (1.M)$$

$$0 = 0 \text{ 00000000 } 0 \dots 0 \quad -1.5 = 1 \text{ 01111111 } 10 \dots 0$$

Magnitude of numbers that can be represented is in the range:

$$2^{-126} (1.0) \quad \text{to} \quad 2^{127} (2 - 2^{-23})$$

which is approximately:

$$1.8 \times 10^{-38} \quad \text{to} \quad 3.40 \times 10^{38}$$

Floating Point Complexities

- Operations are somewhat more complicated
- In addition to overflow we can have “underflow”
- Accuracy can be a big problem
 - IEEE 754 keeps two extra bits, guard and round
 - four rounding modes
 - positive divided by zero yields “infinity”
 - zero divide by zero yields “not a number”
 - other complexities
- Implementing the standard can be tricky
- Not using the standard can be even worse
 - see text for description of 80x86 and Pentium bug!

Chapter Four Summary

- Computer arithmetic is constrained by limited precision
- Bit patterns have no inherent meaning but standards do exist
 - two’s complement
 - IEEE 754 floating point
- Computer instructions determine “meaning” of the bit patterns
- Performance and accuracy are important so there are many complexities in real machines (i.e., algorithms and implementation).
- Next class: floating pt arithmetic, rounding
- After that we are ready to move on (and implement the processor)