

# CS 211: Project 4 Discussion

Chris Kauffman

Week 8, 9

# Front Matter

## Today

- ▶ Discuss P4
- ▶ Finish Interfaces
- ▶ Exceptions

## Lab 9: Quiz

- ▶ Enumerations, Abstract Classes, Interfaces
- ▶ Will put up practice problems tomorrow

## P4: GateSim

- ▶ Due ~ 2 weeks
- ▶ Walk-through circuit creation
- ▶ Field Questions

# Gates

- ▶ What makes computers compute
- ▶ Typically have 1-2 inputs, 1 output
- ▶ Signals for Input/Output: HI, LO, X
- ▶ Generalize to multiple inputs

# Circuits

- ▶ Comprised of gates
- ▶ Inputs / Outputs defined by Connector
- ▶ Specified in text files

## Circuits can be Composed

```
halfadder.txt:
```

```
-----  
A B -> carry sum  
  
AND A B -> carry  
XOR A B -> sum
```

```
fulladder.txt:
```

```
-----  
IMPORT halfadder  
  
X Y C_in -> C_out Sum  
  
halfadder X Y -> C1 S1  
halfadder C_in S1 -> C2 Sum  
OR C1 C2 -> C_out
```

- ▶ Fabulous property that allows circuits to use other circuits
- ▶ Allows abstractions to be built up
- ▶ Involves a mild level of recursion: while parsing a circuit file, may need to open up another circuit file
- ▶ Do this in a week or two

## Majority Circuit: Memory Diagram

Walk through the memory diagram of Circuit for processing

- ▶ **Fields of Circuit?**
- ▶ Wires and Gate/Logic elements
- ▶ Illustrate file processing


A B C -> maj

AND A B -> a1

AND A C -> a2

AND B C -> a3

OR a1 a2 a3 -> maj

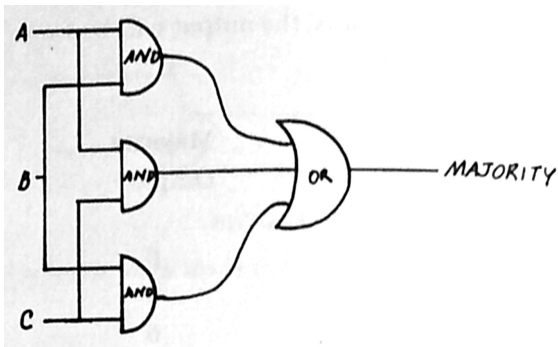

## Another Possible Example

Circuit XOR: same output as an XOR gate without using one

A B -> out

NOT A -> notA

NOT B -> notB

AND A notB -> temp1

AND notA B -> temp2

OR temp1 temp2 -> out